

LAB-4 Assignment

Design the circuit given below by using IPs and show the results on Basy3 board.

